

# Homework 2

2023.07.13 沈韵涵 3200104392

## Chap 2

**2.40** Write the decimal equivalents for these IEEE floating point numbers.

- a. 0 10000000 000000000000000000000000
- b. 1 10000011 000100000000000000000000
- c. 0 11111111 000000000000000000000000
- d. 1 10000000 100100000000000000000000

a.

$$\begin{aligned} \text{Sign} &= 0 \\ \text{Exp} &= (1000\ 0000)_B - 127_D = 128 - 127 = 1 \\ \text{Frac} &= 1.0 \\ \therefore N_a &= (-1)^0 * 1.0 * 2^1 = 2.0 \end{aligned}$$

b.

$$\begin{aligned} \text{Sign} &= 1 \\ \text{Exp} &= (1000\ 0011)_B - 127_D = 4 \\ \text{Frac} &= 1.0001_B = 1\frac{1}{16} = 1.0625 \\ \therefore N_b &= (-1)^1 * 1.0625 * 2^4 = -17 \end{aligned}$$

c.

$$\begin{aligned} \therefore \begin{cases} \text{Sign} = 0 \\ \text{Exp containing all 1's} \\ \text{Frac containing all 0's} \end{cases} \\ \therefore N_c &= \text{Positive Infinity} \end{aligned}$$

d.

$$\begin{aligned} \text{Sign} &= 1 \\ \text{Exp} &= (1000\ 0000)_B - 127_D = 1 \\ \text{Frac} &= 1.1001_D = 1\frac{25}{16} = 1.5625 \\ \therefore N_d &= (-1)^1 * 1.5625 * 2^1 = -3.125 \end{aligned}$$

**2.48** Convert the following decimal numbers to hexadecimal representations of 2's complement numbers.

- a. 256
- b. 111
- c. 123,456,789
- d. -44

a.

$$\begin{aligned} 256 &= 0000\ 0001\ 0000\ 0000(2's\ complement) \\ &= 0100(hexadecimal) \end{aligned}$$

b.

$$\begin{aligned} 111 &= 0110\ 1111(2's\ complement) \\ &= 6F(hexadecimal) \end{aligned}$$

c.

$$\begin{aligned} 123456789 &= 0000\ 01111\ 0101\ 1100\ 1101\ 0001\ 0101(2's\ complement) \\ &= 075B\ CD15(hexadecimal) \end{aligned}$$

d.


$$\begin{aligned} &\begin{cases} 44 = 0010\ 1100 \\ \overline{44} = 1101\ 0011 \\ \overline{44} + 1 = 1101\ 0100 \end{cases} \\ \therefore -44's\ 2's\ complement &= 1101\ 0100 \\ it's\ hexadecimal &= D4 \end{aligned}$$

## Chap 3

---

**3.6** For the transistor-level circuit in Figure 3.38, fill in the truth table. What is  $Z$  in terms of  $A$  and  $B$ ?

$A$	$B$	$C$	$D$	$Z$

 

**Figure 3.38** Diagram for Exercise 3.6.

- The truth table:

$A$	$B$	$C$	$D$	$Z$
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

$$Z = \overline{C} \cdot \overline{D} = \overline{\overline{A}} \cdot \overline{\overline{B}} = A \cdot B (A \text{ and } B)$$

### 3.20 How many output lines will a 16-input multiplexer have? How many select lines will this multiplexer have?

Since the multiplexer has 16 input &  $\log_2(16) = 4$ , it could have:

- ONLY ONE output line.
- 4 select lines.

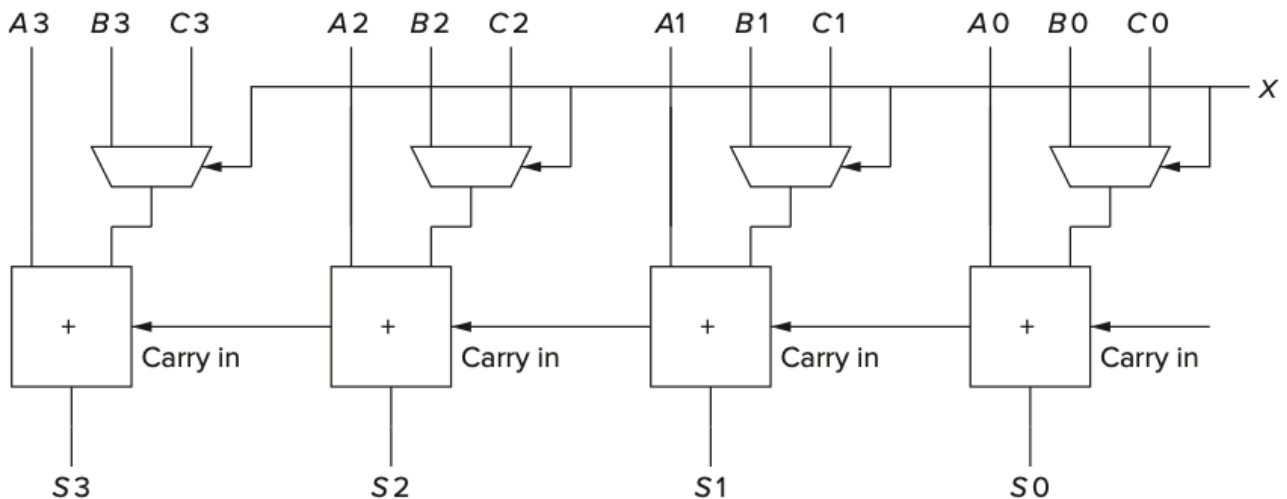



Figure 3.42 Diagram for Exercise 3.30.

- 3.30** a. Figure 3.42 shows a logic circuit that appears in many of today's processors. Each of the boxes is a full-adder circuit. What does the value on the wire  $X$  do? That is, what is the difference in the output of this circuit if  $X = 0$  vs. if  $X = 1$ ?
- b. Construct a logic diagram that implements an adder/subtractor. That is, the logic circuit will compute  $A + B$  or  $A - B$  depending on the value of  $X$ . *Hint:* Use the logic diagram of Figure 3.42 as a building block.

a.

$$\begin{cases} X = 0 \Rightarrow output = A + B \\ X = 1 \Rightarrow output = A + C \end{cases}$$


b.

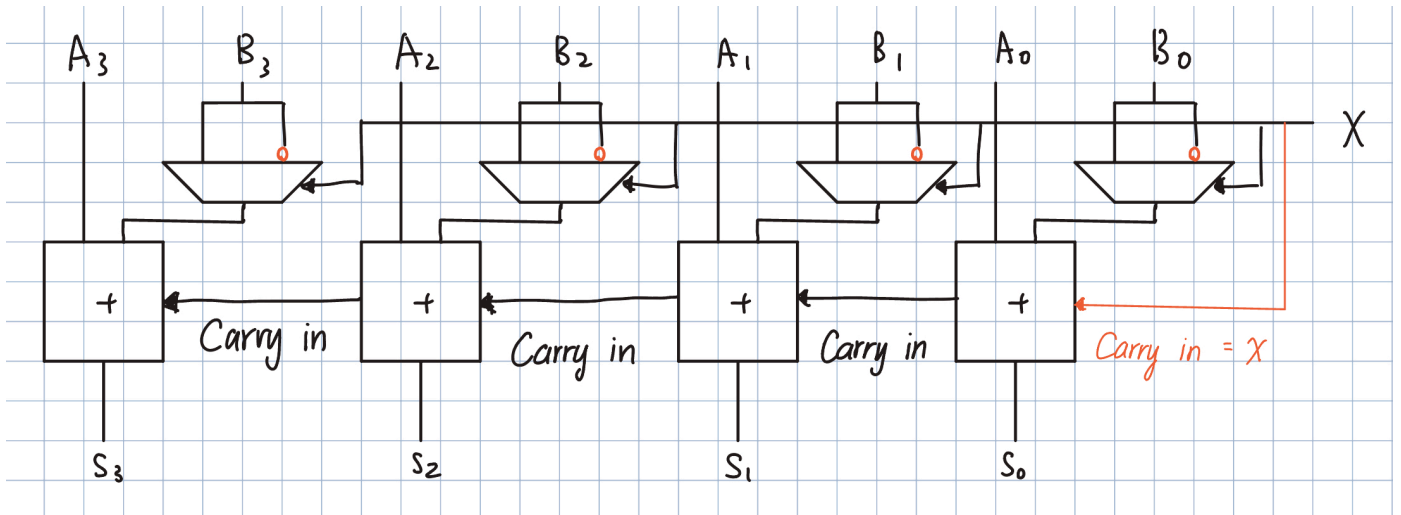





$$\begin{cases} X = 0 \Rightarrow \text{output} = A + B \\ X = 1 \Rightarrow \text{output} = A + (\overline{B} + 1) = A + (-B) = A - B \end{cases}$$

**3.36** A comparator circuit has two 1-bit inputs  $A$  and  $B$  and three 1-bit outputs  $G$  (greater),  $E$  (Equal), and  $L$  (less than). Refer to Figures 3.43 and 3.44 for this problem.

$G$  is 1 if  $A > B$        $E$  is 1 if  $A = B$        $L$  is 1 if  $A < B$   
 0 otherwise              0 otherwise              0 otherwise

 

**Figure 3.43** Diagram for Exercise 3.36.

    

————→ EQUAL

**Figure 3.44** Diagram for Exercise 3.36.

a. Draw the truth table for a one-bit comparator.

<i>A</i>	<i>B</i>	<i>G</i>	<i>E</i>	<i>L</i>
0	0			
0	1			
1	0			
1	1			


b. Implement *G*, *E*, and *L* using AND, OR, and NOT gates.

c. Using the one-bit comparator as a basic building block, construct a four-bit equality checker such that output EQUAL is 1 if  $A_{3:0} = B_{3:0}$ , 0 otherwise.

a. The truth table:


A	B	G	E	L
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	1

b.

 


C.



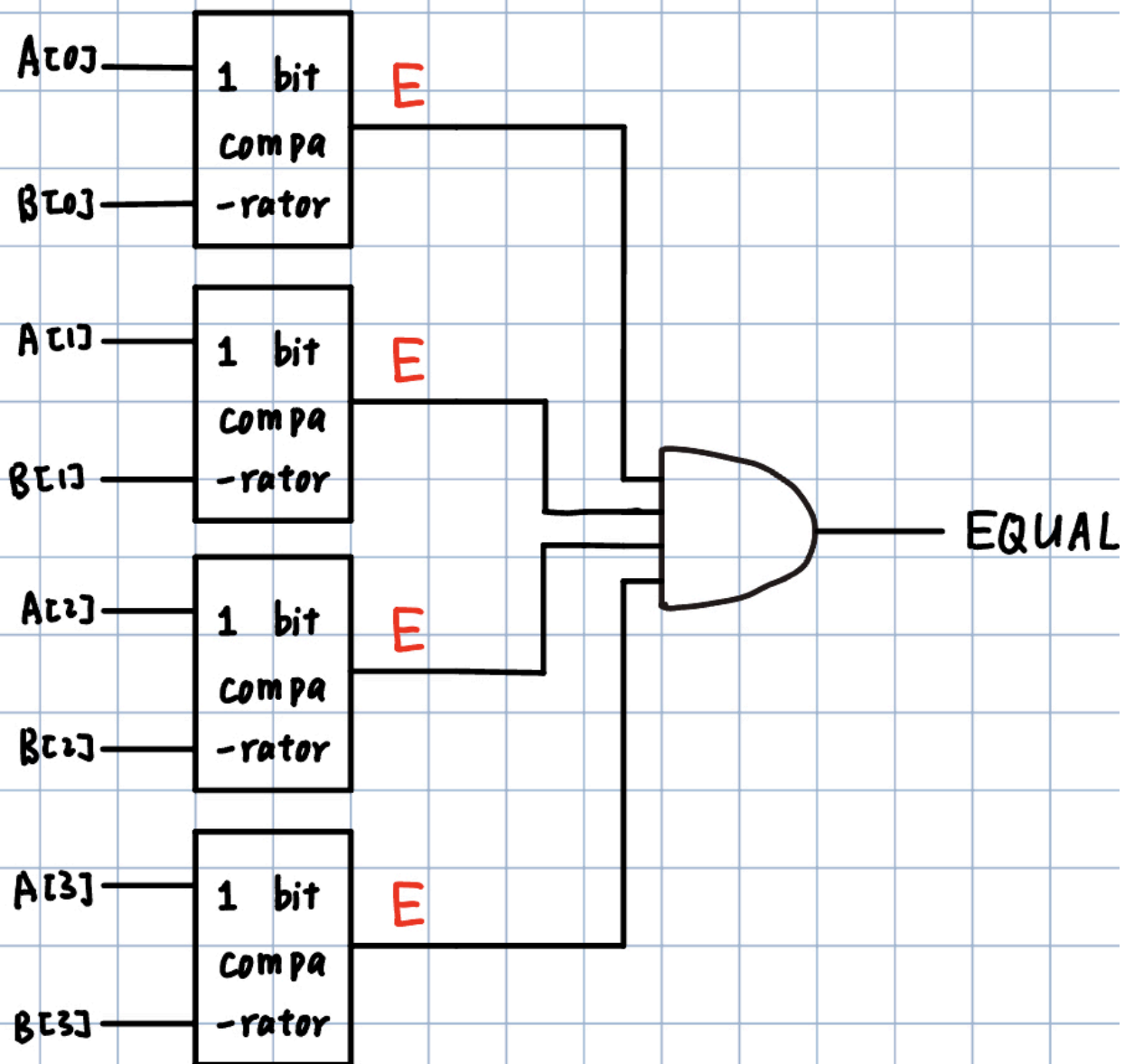

3.40 For the memory shown in Figure 3.45:

- What is the address space?
- What is the addressability?
- What is the data at address 2?

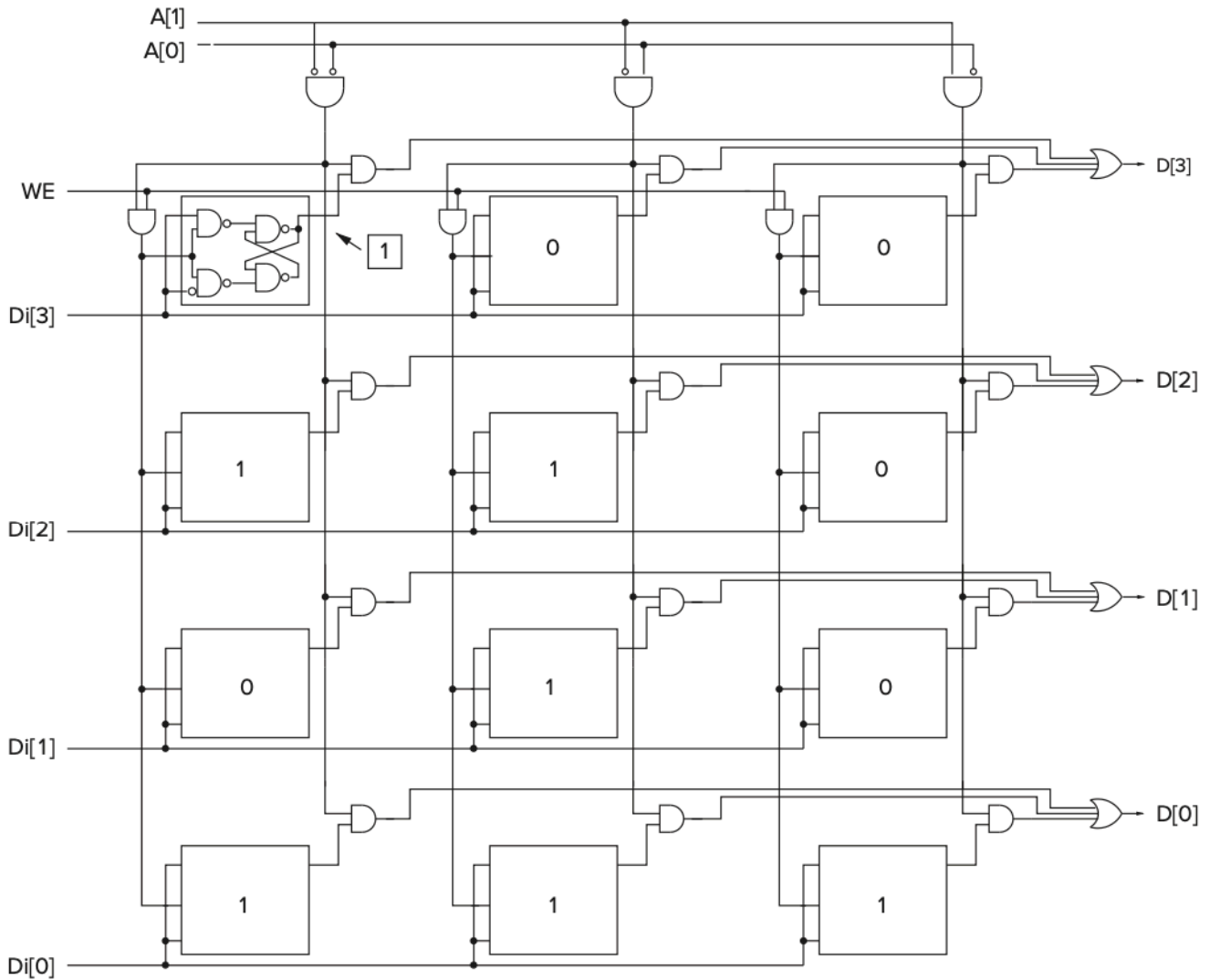

**Figure 3.45** Diagram for Exercise 3.40.

- According to Figure 3.45 the memory uses 2-bit ( $A[1]$  &  $A[0]$ ) address, thus it's  $address\_space = 2^2 = 4$
- Since each memory location stores 4-bits( $D[3:0]$ ), it's  $addressability = 4$
- Since  $address(2) = 10_B$ , we could find that  $data\ at\ address(2) = 0001$

**3.50** Prove that the NAND gate, by itself, is logically complete (see Section 3.3.5) by constructing a logic circuit that performs the AND function, a logic circuit that performs the NOT function, and a logic circuit that performs the OR function. Use only NAND gates in these three logic circuits.

$$\therefore \begin{cases} NOT = \overline{X} = \overline{X} + \overline{X} = \overline{X \cdot X} & (1) \\ OR = X + Y = \overline{\overline{X} \cdot \overline{Y}} = \overline{\overline{X} \cdot \overline{Y} \cdot \overline{Y}} & (2) \\ AND = X \cdot Y = \overline{\overline{X \cdot Y}} = \overline{\overline{X} \cdot \overline{Y}} & (3) \end{cases} \quad (4)$$

and  $Set\{AND, OR, NOT\}$  is logically complete

$\therefore$  NAND is also logically complete

The logical circuits are as follows:

